

Ch32 (Homework)**Current Score :** - / 27**Due :** Monday, August 27 2018 02:30 PM CDT

1. -/2 points SerPSE9 32.P.004.MI.FB.

A solenoid of radius **1.70** cm has **440** turns and a length of **25.0** cm.

(a) Find its inductance.

 mH

(b) Find the rate at which current must change through it to produce an emf of **70.0** mV.

(Enter the magnitude.)

 A/s**Need Help?**[Read It](#)[Master It](#)

2. -/4 points SerPSE9 32.P.006.

A **36.5** mA current is carried by a uniformly wound air-core solenoid with **400** turns, a **16.5** mm diameter, and **11.5** cm length.

(a) Compute the magnetic field inside the solenoid.

 μT

(b) Compute the magnetic flux through each turn.

 $\text{T}\cdot\text{m}^2$

(c) Compute the inductance of the solenoid.

 mH

(d) Which of these quantities depends on the current? (Select all that apply.)

- magnetic field inside the solenoid
- magnetic flux through each turn
- inductance of the solenoid

Need Help?[Read It](#)

3. -/3 points SerPSE9 32.P.009.WI.

The current in a 70.0-mH inductor changes with time as $i = 3.00t^2 - 7.00t$, where i is in amperes and t is in seconds.

(a) Find the magnitude of the induced emf at $t = 1.00$ s.

mV

(b) Find the magnitude of the induced emf at $t = 4.00$ s.

mV

(c) At what time is the emf zero?

s


Need Help?

Read It

Watch It

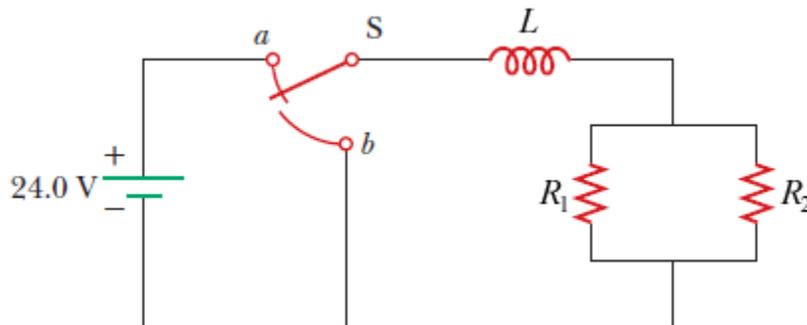4. -/2 points SerPSE9 32.P.019.

Consider the circuit shown in the figure below where $L = 4.65$ mH and $R_2 = 445$ Ω .



(a) When the switch is in position a , for what value of R_1 will the circuit have a time constant of 14.9 μs ?

k Ω

(b) What is the current in the inductor at the instant the switch is thrown to position b ?


mA

Need Help?

Read It

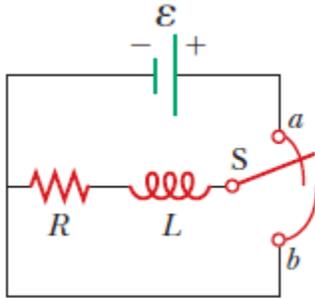5. -/3 points SerPSE9 32.P.031.MI.

A 140-mH inductor and a 5.20- Ω resistor are connected with a switch to a 6.00-V battery as shown in the figure below.



(a) After the switch is first thrown to a (connecting the battery), what time interval elapses before the current reaches 220 mA?

ms

(b) What is the current in the inductor 10.0 s after the switch is closed?

A

(c) Now the switch is quickly thrown from a to b . What time interval elapses before the current in the inductor falls to 160 mA?

ms

Need Help?

Read It

Master It

6. -/2 points SerPSE9 32.P.035.

On a clear day at a certain location, a 147-V/m vertical electric field exists near the Earth's surface. At the same place, the Earth's magnetic field has a magnitude of 4.500×10^{-5} T.

(a) Compute the energy density of the electric field.

nJ/m³

(b) Compute the energy density of the magnetic field.

μ J/m³

Need Help?

Read It

7. -/2 points SerPSE9 32.P.039.

The magnetic field inside a superconducting solenoid is 4.90 T. The solenoid has an inner diameter of 6.20 cm and a length of 26.0 cm.

(a) Determine the magnetic energy density in the field.

$$u_B = \boxed{} \text{ J/m}^3$$

(b) Determine the energy stored in the magnetic field within the solenoid.

$$U_B = \boxed{} \text{ kJ}$$

Need Help?

Read It

8. -/1 points SerPSE9 32.P.041.

Two coils, held in fixed positions, have a mutual inductance of $130 \mu\text{H}$. What is the peak emf in one coil when the current in the other coil is $i(t) = 15.0 \sin(1.25 \times 10^3 t)$, where i is in amperes and t is in seconds?

$$\boxed{} \text{ V}$$


Need Help?

Read It

9. -/1 points SerPSE9 32.P.045.

On a printed circuit board, a relatively long, straight conductor and a conducting rectangular loop lie in the same plane as shown in the figure below. Taking $h = 0.400$ mm, $w = 1.10$ mm, and $\ell = 2.70$ mm, find their mutual inductance.

$$\boxed{} \text{ pH}$$

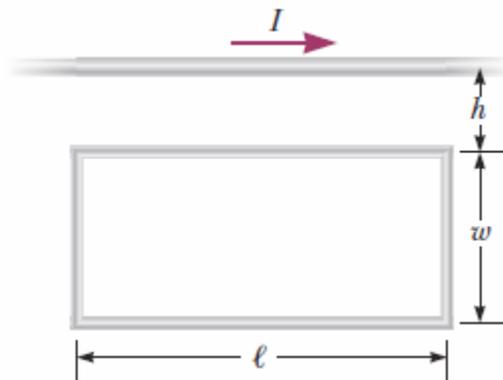


Need Help?

Read It

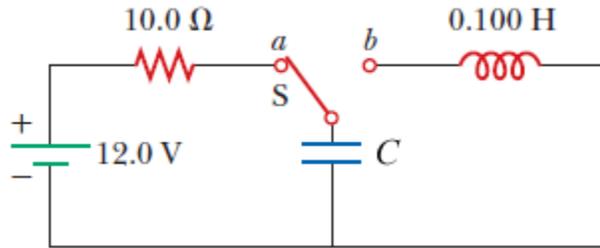10. -/4 points SerPSE9 32.P.053.WI.

The switch in the figure below is connected to position *a* for a long time interval. At $t = 0$, the switch is thrown to position *b*. After this time, what are the following? (Let $C = 1.10 \mu\text{F}$.)



(a) the frequency of oscillation of the *LC* circuit

Hz

(b) the maximum charge that appears on the capacitor

μC

(c) the maximum current in the inductor

mA

(d) the total energy the circuit possesses at $t = 3.00 \text{ s}$

μJ


Need Help?

Read It

Watch It

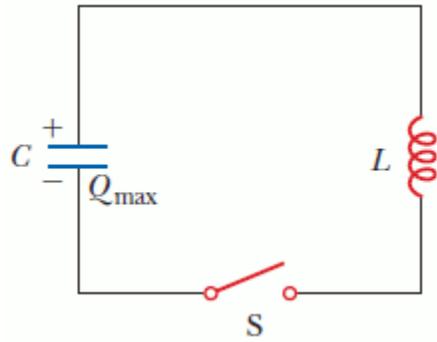11. -/3 points SerPSE9 32.P.054.

An LC circuit like that in the figure below consists of a 3.30-H inductor and an 838-pF capacitor that initially carries a 128- μC charge. The switch is open for $t < 0$ and is then thrown closed at $t = 0$. Compute the following quantities at $t = 4.00$ ms.



(a) the energy stored in the capacitor

J

(b) the total energy in the circuit

J

(c) the energy stored in the inductor

J

Need Help?

[Read It](#)